

Alternating Current


Phasor and Alternating Current





$$v = V_{\max} \cos \omega t$$

$$i = I_{\max} \cos \omega t$$

phasor diagram

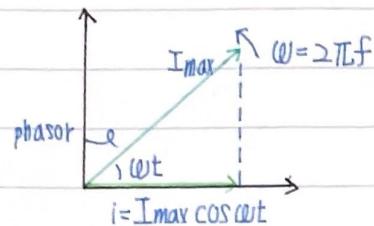

rectified alternating current

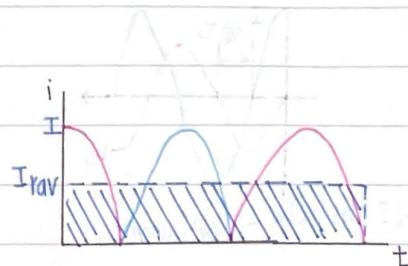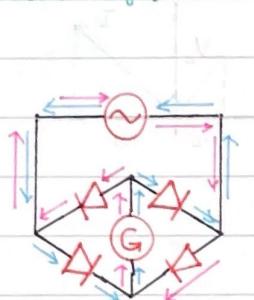

$$I_{\text{rect}} = |\cos \omega t|_{\text{av}} I = \frac{2}{\pi} I$$

root-mean-square current

$$i = I_{\max} \cos \omega t, \quad i^2 = I_{\max}^2 \cos^2 \omega t \\ = I_{\max}^2 \frac{1}{2} (1 + \cos 2\omega t)$$

$$= \frac{1}{2} I_{\max}^2 + \frac{1}{2} I_{\max}^2 \cos 2\omega t$$

$$\langle i^2 \rangle = \left\langle \frac{1}{2} I_{\max}^2 \right\rangle + \left\langle \frac{1}{2} I_{\max}^2 \cos 2\omega t \right\rangle = \frac{1}{2} I_{\max}^2$$



$$I_{\text{rms}} = \frac{I}{\sqrt{2}}$$

$$P_{\text{avg}} = I_{\text{rms}}^2 R$$

$$V_{\text{rms}} = \frac{V}{\sqrt{2}}$$

Resistance and Reactance


resistor in an AC circuit

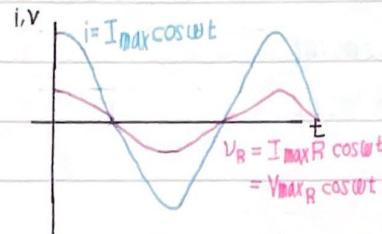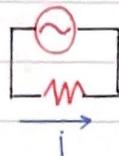




$$v_R = IR = I R \cos \omega t$$

$$V_{maxR} = I_{max} R$$

$$v_R = V_{maxR} \cos \omega t$$

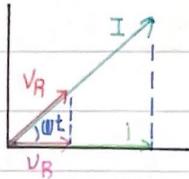

inductor in an AC circuit

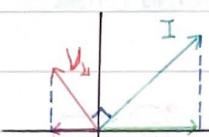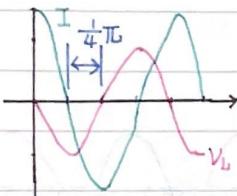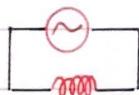

$$V_L = L \frac{di}{dt} = L \frac{d}{dt}(I \cos \omega t) = -I \omega L \sin \omega t$$

$$= I \omega L \cos(\omega t + 90^\circ)$$


$$= V_{maxL} \cos(\omega t + \phi), V_{maxL} = I \omega L, \text{ for pure inductor, } \phi = 90^\circ$$

$$\text{inductive reactance } X_L = \omega L$$

$$\Rightarrow V_{maxL} = I_{max} X_L$$

when $\omega \uparrow$ or $L \uparrow$, $X_L \uparrow$, $I_{max} \downarrow$: low-pass filter

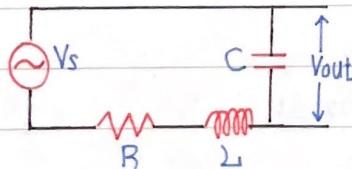
$$V_{out} = V_C = \frac{1}{\omega C}, \frac{V_{out}}{V_s} = \frac{1}{\omega C \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$



$$\text{if } \omega \text{ is large, } \frac{V_{out}}{V_s} = \frac{1}{\omega C (\omega L)^2} = \frac{1}{L C \omega^2}$$


$$\text{if } \omega \text{ is small, } \frac{V_{out}}{V_s} = \frac{1}{\omega C (\frac{1}{\omega C})^2} = \frac{\omega C}{\omega C} = 1$$

The L-R-C Parallel Circuit

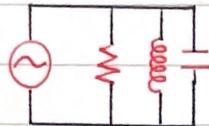

$$V = V_R = V_L = V_C$$

$$I = i_R + i_L + i_C$$

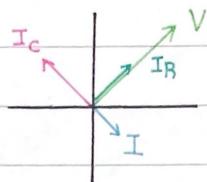

$$I^2 = I_R^2 + (I_C - I_L)^2 = \left(\frac{V}{R}\right)^2 + \left(V\omega C - \frac{V}{\omega L}\right)^2$$

$$I = \sqrt{\frac{1}{R^2} + (\omega C - \frac{1}{\omega L})^2}$$

large ω , $\Rightarrow \frac{1}{\omega L}$ the current in the capacitor branch is much larger

small ω , $\Rightarrow \omega L$ the current in the inductive branch is much larger

Power in Alternating- Current Circuits

power in resistor


$$P_{av} = \frac{1}{2} VI = \frac{V}{\sqrt{2}} \frac{I}{\sqrt{2}} = V_{rms} I_{rms} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

power in inductor

$$P_{av} = 0$$

power in capacitor

$$P_{av} = 0$$

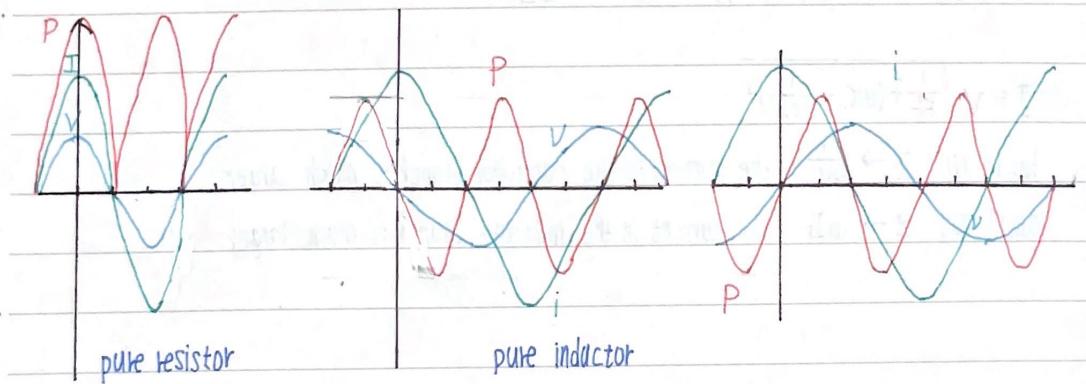

$$\begin{aligned} P_{av} &= \langle P \rangle = \langle [V(\cos\omega t + \phi)][I \cos\omega t] \rangle \\ &= \langle V_{max} (\cos\omega t \cos\phi - \sin\omega t \sin\phi) I_{max} \cos\omega t \rangle \\ &= \langle V_{max} I_{max} \cos\phi \frac{\cos^2\omega t}{2} - V_{max} I_{max} \sin\phi \frac{\cos\omega t \sin\omega t}{2} \rangle \end{aligned}$$

$$= \frac{1}{2} V_{max} I_{max} \cos\phi$$

$$= V_{rms} I_{rms} \cos\phi \quad \text{power factor}$$

for a pure resistance, $\phi = 0$


pure inductor or capacitor, $\phi = \pm 90^\circ$

L-R-C series

$$\cos\phi = \frac{R}{Z}$$

2023-08-11

Capacitor in an AC circuits

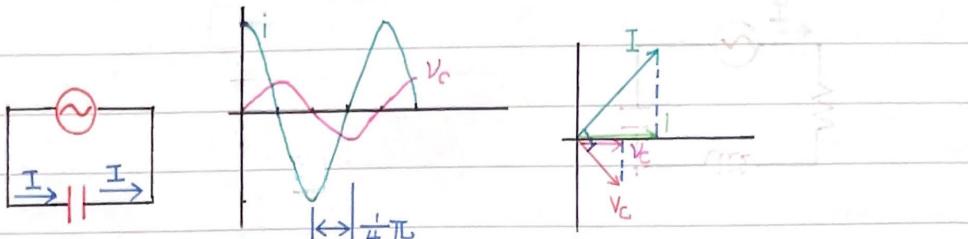


$$i = \frac{d\theta}{dt} = I \cos \omega t, \quad \theta = \frac{I}{\omega} \sin \omega t$$


$$v_c = \frac{\theta}{C} = \frac{I}{\omega C} \sin \omega t = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$$

$$V_{maxc} = \frac{1}{\omega C} \quad \text{capacitive reactance } X_C = \frac{1}{\omega C}$$

$$V_{maxc} = I X_C$$

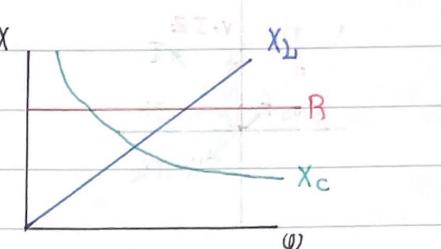

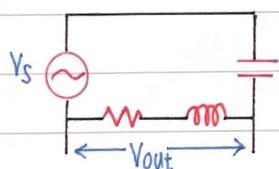when $\omega \uparrow$ or $C \uparrow$, $X_C \downarrow$, $I_{max} \uparrow$: high-pass filter



$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}, \quad I = \frac{V_s}{Z} = \frac{V_s}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$V_{out} = I \sqrt{R^2 + X_L^2} = I \sqrt{R^2 + \omega^2 L^2} = V_s \sqrt{\frac{R^2 + \omega^2 L^2}{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \frac{V_{out}}{V_s} = \sqrt{\frac{R^2 + \omega^2 L^2}{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$




$$\omega \text{ small: } \frac{V_{out}}{V_s} \rightarrow \sqrt{\frac{R^2}{\omega^2 C^2}} = \omega RC$$

$$\omega \text{ large: } \frac{V_{out}}{V_s} \rightarrow \sqrt{\frac{\omega^2 L^2}{\omega^2 L^2}} = 1$$

NO.

DATE / /

The L-R-C Series Circuit

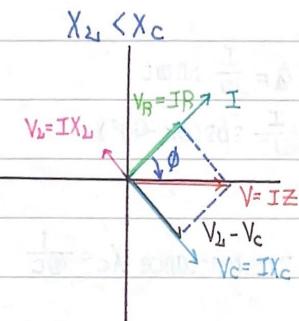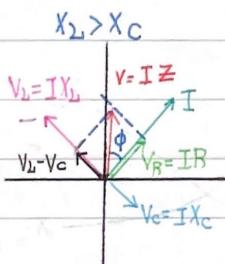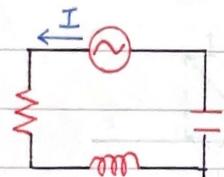

$$V_R = IR \quad V_L = IX_L \quad V_C = IX_C$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(IR)^2 + (IX_L - IX_C)^2} = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{Impedance } Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\Rightarrow V = IZ$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{I(X_L - X_C)}{IR} = \frac{X_L - X_C}{R} = \frac{\omega L - \frac{1}{\omega C}}{R}$$



$$\frac{V}{\sqrt{2}} = \frac{I}{\sqrt{2}} Z, \quad V_{rms} = I_{rms} Z$$

Resonance in AC Circuits

at resonance

$$X_L = X_C \quad \omega_0 L = \frac{1}{\omega_0 C}, \quad \omega_0 = \sqrt{LC} \quad f_0 = \frac{\omega_0}{2\pi}$$

R, X, Z

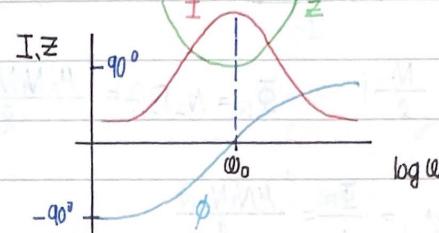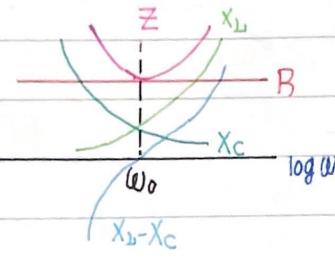


$$P_{avg} = I_{rms}^2 R = \frac{(\Delta V_{rms})^2}{Z^2} R = \frac{(\Delta V_{rms})^2 R}{R^2 + (X_L - X_C)^2} = \frac{(\Delta V_{rms})^2 R}{R^2 (\omega^2 + L^2/C^2)} = \frac{(\Delta V_{rms})^2 R \omega^2}{R^2 \omega^2 + L^2 (\omega^2 - \omega_0^2)^2}$$

$$= \frac{(\Delta V_{rms})^2 R \omega^2}{R^2 \omega^2 + L^2 (\omega^2 - \omega_0^2)^2}$$

when L and C fixed

I

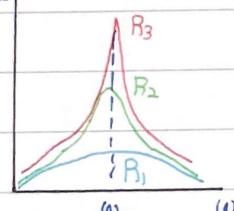

$R_1 > R_2 > R_3$

curve sharpness described by quality factor, Q


$$Q = \frac{\omega_0}{\Delta \omega} = \frac{\omega_0}{B}$$

width of the curve measured between the two values of ω for which P_{avg} at half-power points

NO.

DATE / /

Transformers

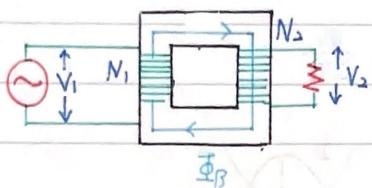

$$\mathcal{B} = \mu_0 \frac{N_1}{l} i \quad \Phi_B = N_2 \mathcal{B} A = \frac{\mu_0 N_1 N_2 A i}{l}$$

$$M_{12} = M_{21} = \frac{\Phi_B}{i} = \frac{\mu N_1 N_2 A}{l}$$

$$\mathcal{L}_{11} = \mu_0 \left(\frac{N_1}{l} \right)^2 A \cdot l = \frac{\mu N_1^2 A}{l} \quad \mathcal{L}_{22} = \mu \left(\frac{N_2}{l} \right)^2 A \cdot l = \frac{\mu N_2^2 A}{l}$$

$$K = \frac{M}{\sqrt{\mathcal{L}_{11} \mathcal{L}_{22}}} \quad \text{When } K \leq 1, \text{ magnetic leakage}$$

$$\mathcal{E}_1 = -N_1 \frac{d\Phi_B}{dt} \quad \mathcal{E}_2 = -N_2 \frac{d\Phi_B}{dt} \Rightarrow \frac{\mathcal{E}_1}{\mathcal{E}_2} = \frac{N_1}{N_2}$$

$$V_1 I_1 = V_2 I_2, \quad I_2 = \frac{V_2}{R}$$

$$\frac{V_1}{I_1} = \frac{R}{\left(\frac{N_2}{N_1}\right)^2}$$