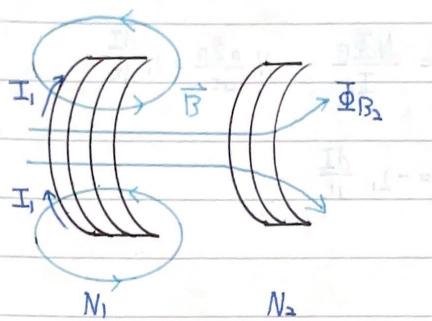


Inductance

Mutual Inductance



do you know what is?

coil 1 has current I1

coil 2 has current I2

$$\Phi_{B2} = \int \vec{B}_1 \cdot d\vec{A}_2 \text{ and } \Phi_{B2} \propto I_1, N_2 \Phi_{B2} = M_{21} I_1, M: \text{proportionality constant}$$

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{B2}}{dt} = M_{21} \frac{dI_1}{dt}, M_{21} = \frac{N_2 \Phi_{B2}}{I_1}$$

$$\Phi_{B1} = \int \vec{B}_2 \cdot d\vec{A}_1, N_1 \Phi_{B1} = M_{12} I_2$$

$$\mathcal{E}_1 = -N_1 \frac{d\Phi_{B1}}{dt} = M_{12} \frac{dI_2}{dt}, M_{12} = \frac{N_1 \Phi_{B1}}{I_2}$$

if the coils are in a vacuum, the flux Φ_B through each turn of coil is directly proportional to the current I

in this discussion we will assume that any magnetic material present has constant K_m so


that $\Phi \propto I$ and M_{21} depends on geometry only

M_{21} is always equal to M_{12}

$$[M] = [N] \frac{[\Phi_B]}{[I]} = \frac{\text{Wb}}{\text{A}} = \frac{\text{V} \cdot \text{s}}{\text{A}} = \text{Oe} \cdot \text{s} = \frac{\text{T}}{\text{A}^2} = \text{H}$$

Self-Inductance and Inductors


self-inductance

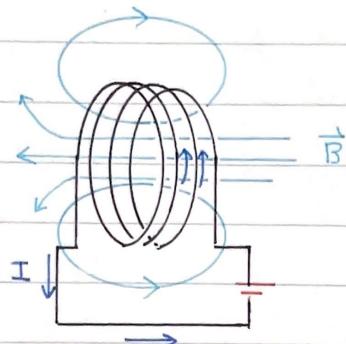

$$L = \frac{N\Phi_B}{I} = N \frac{d\Phi_B}{dt} = L \frac{di}{dt}$$

$$E = -L \frac{di}{dt}$$

inductor

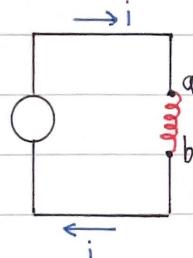


conservative field \vec{E}_c non conservative field \vec{E}_n

$$\vec{E}_{\text{total}} = \vec{E}_c + \vec{E}_n = \vec{0}$$

$$\oint \vec{E}_n \cdot d\vec{l} = -L \frac{di}{dt} = \int_a^b \vec{E}_n \cdot d\vec{l}, \text{ so that } \int_a^b \vec{E}_c \cdot d\vec{l} = L \frac{di}{dt}$$

$$V_a - V_b = L \frac{di}{dt} = V_{ab}$$

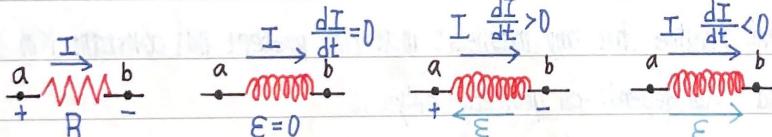

$$V_{ab} = IR > 0$$

$$V_{ab} = L \frac{di}{dt} = 0$$

$$V_{ab} = L \frac{di}{dt} > 0$$



$$V_{ab} = L \frac{di}{dt} < 0$$

in the following examples, we will assume that the circuit encloses only vacuum

an added complication is that with ferromagnetic materials the magnetization is in

general not a linear function of magnetizing current, in our discussion we will ignore this complication and assume always that the inductance is constant


toroidal solenoid I

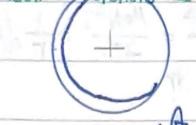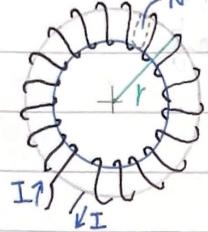assume B is uniform across a cross section

$$B = \mu_0 \frac{NI}{2\pi r} \quad \Phi_B = BA = \frac{\mu_0 NI A}{2\pi r}$$

$$L = N \frac{\Phi_B}{I} = \frac{\mu_0 N^2 A}{2\pi r}$$

coaxial cable

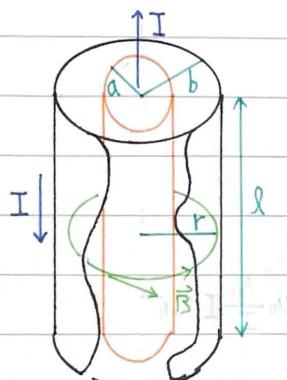

$$B = \frac{\mu_0 I}{2\pi r} \quad d\Phi_B = B dA = B l dr$$


$$\Phi_B = \int_a^b \frac{\mu_0 I}{2\pi r} l dr$$

$$= \frac{\mu_0 I l}{2\pi} \int_a^b \frac{dr}{r}$$

$$= \frac{\mu_0 I l}{2\pi} \ln \frac{b}{a}$$

$$L = \frac{\Phi_B}{I}$$
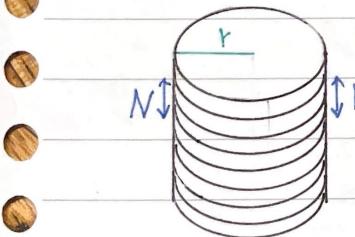
$$= \frac{\mu_0 l}{2\pi} \ln \frac{b}{a}$$




$$B = \mu_0 NI$$

$$\Phi_B = \mu_0 NI \cdot N \cdot \pi r^2 = \mu_0 N^2 \pi r^2 I$$


$$L = \frac{\Phi_B}{I} = \mu_0 N^2 \pi r^2$$

torodial solenoid II

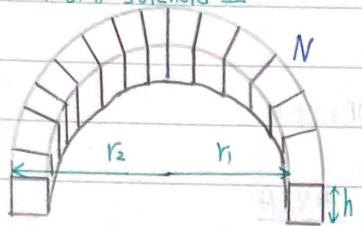

$$\begin{aligned} B &= \frac{\mu_0 N I}{2\pi r} & \Phi_B &= N \int_S \vec{B} \cdot d\vec{A} = \frac{\mu_0 N^2 I}{2\pi} \int_{r_1}^{r_2} \frac{1}{r} dr \\ r < r < r_2 & & &= \frac{\mu_0 N^2 I h}{2\pi} \ln \frac{r_2}{r_1} \\ & & &= \frac{\mu_0 N^2 I h}{2\pi} \ln \frac{r_2}{r_1} \end{aligned}$$
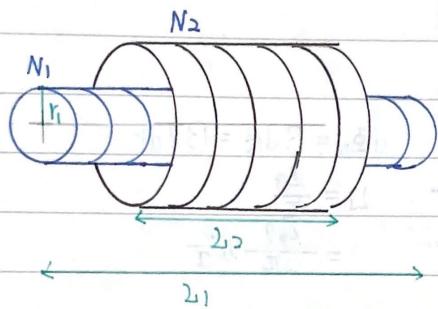
$$\Sigma = \frac{\Phi_B}{I} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{r_2}{r_1}$$



$$B = \mu_0 N I = \mu_0 \frac{N_1}{L_1} I \quad \Phi_B = \frac{N_2 \int \vec{B} \cdot d\vec{A}}{L_2} = \frac{N_2}{L_2} \mu_0 \frac{N_1}{L_1} I \pi r_1^2$$

$$M = \frac{\mu_0 N_1 N_2 \pi r_1^2}{L_1 L_2}$$

Magnetic-Field Energy

$$P = V_{ab} I = L I \frac{dI}{dt}, \quad dU = P dt = L I dI$$

$$U = \int P dt = \int_0^I L I dI = L \int_0^I I dI \\ = \frac{1}{2} L I^2$$

Toroidal solenoid I


assume the cross-sectional area A is small enough that we can pretend that the magnetic field is uniform over the area

$$L = \frac{\mu_0 N^2 A}{2\pi r} \quad U = \frac{1}{2} L I^2 = \frac{\mu_0 N^2 A}{4\pi r} I^2$$



$$\text{energy per unit volume, magnetic energy density, } u = \frac{U}{2\pi r A} = \frac{\mu_0}{2} \frac{N^2 I^2}{4\pi^2 r^2} \text{ and } B = \frac{\mu_0 N I}{2\pi r} \\ = \frac{B^2}{2\mu_0} \\ = \frac{B^2}{2\mu} \text{ when the material inside the toroid is not vacuum}$$

$$I: 0 \rightarrow I$$

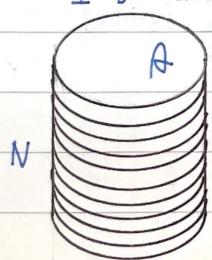

$$B = \mu_0 N I \quad \Phi = nLB A = LI$$

$$P = \frac{dW}{dt} = -I \epsilon = I \frac{d\Phi_B}{dt} = I \frac{d}{dt} LI, \quad dW = LI dt$$

$$W = \int dW = \int_0^I LI dt = \frac{1}{2} LI^2 = U$$

$$U = \frac{\Phi}{I} = \frac{nLB A}{I}, \quad I = \frac{B}{\mu_0 N}$$

$$U = \frac{1}{2} \frac{nLB A}{I} I^2 = \frac{1}{2} nLB A \frac{B}{\mu_0 N} = \frac{1}{2\mu_0} B^2 A L$$

$$U = \frac{L}{A} \frac{B^2}{2\mu_0}$$

NO.

DATE / /

torodial solenoid II

$$B = \frac{\mu_0 NI}{2\pi r} \quad r_1 < r < r_2 \quad U = \frac{\vec{B} \cdot \vec{B}}{2\mu_0} = \frac{1}{2\mu_0} \frac{\mu_0^2 N^2 I^2}{4\pi r^2}$$

$$\begin{aligned} U &= \int_{r_1}^{r_2} U \cdot 2\pi rh dr = 2\pi h \frac{\mu_0^2 N^2 I^2}{2\mu_0 4\pi^2} \int_{r_1}^{r_2} \frac{r dr}{r^2} \\ &= \frac{\mu_0 h N^2 I^2}{4\pi} \ln \frac{r_2}{r_1} = \frac{1}{2} L I^2 \\ \Rightarrow L &= \frac{\mu_0 h N^2}{2\pi} \ln \frac{r_2}{r_1} \end{aligned}$$

(i) $\Gamma_1: 0 \rightarrow I_1, \Gamma_2: I_2 = 0$

$$\frac{dW_{11}}{dt} = I_1 L_{11} \frac{dI_1}{dt}$$

$$W_{11} = \frac{1}{2} L_{11} I_1^2$$

(i) $\Gamma_1: I_1 = 0, \Gamma_2: 0 \rightarrow I_2$

$$W_{22} = \frac{1}{2} L_{22} I_2^2$$

(ii) $\Gamma_2: 0 \rightarrow I_2, \Gamma_1: I_1 \text{ fixed}$

$$\frac{dW_{22}}{dt} = I_2 L_{22} \frac{dI_2}{dt}$$

$$\frac{dW_{21}}{dt} = I_1 L_{21} \frac{dI_2}{dt}$$

$$\int \left(\frac{dW_{22}}{dt} + \frac{dW_{21}}{dt} \right) dt = \frac{1}{2} L_{22} I_2^2 + I_1 L_{21} I_2$$

(ii) $\Gamma_1: 0 \rightarrow I_1, \Gamma_2: I_2 \text{ fixed}$

$$W_{11} = \frac{1}{2} L_{11} I_1^2$$

$$W_{12} = I_1 L_{12} I_1$$



$$W_{11} + W_{22} + W_{21} = \frac{1}{2} L_{11} I_1^2 + \frac{1}{2} L_{22} I_2^2 + I_1 L_{21} I_2 = W_{22} + W_{11} + W_{12} = \frac{1}{2} L_{22} I_2^2 + \frac{1}{2} L_{11} I_1^2$$

$$\Rightarrow W_{21} = W_{12} = I_1 I_2 L_{12} = I_1 I_2 L_{21} + I_2 L_{21} I_1$$

$$\Rightarrow L_{12} = L_{21}$$

The R-L Circuit

current growth

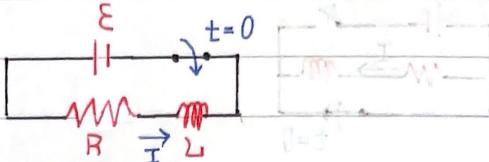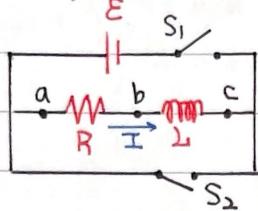


$$V_{ab} = iR \quad V_{bc} = L \frac{di}{dt}$$

$$\mathcal{E} - iR - L \frac{di}{dt} = 0, \quad \frac{di}{dt} = \frac{\mathcal{E} - iR}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L} i$$

$$\frac{di}{i - \frac{\mathcal{E}}{R}} = -\frac{R}{L} dt, \quad \int_0^i \frac{di'}{i' - \frac{\mathcal{E}}{R}} = -\int_0^t \frac{R}{L} dt, \quad \ln \frac{i - \frac{\mathcal{E}}{R}}{\frac{\mathcal{E}}{R}} = -\frac{R}{L} t$$

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-\frac{R}{L} t} \right), \quad \frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-\frac{R}{L} t} \quad t=0 \quad i=0 \quad \frac{di}{dt} = \frac{\mathcal{E}}{L}$$

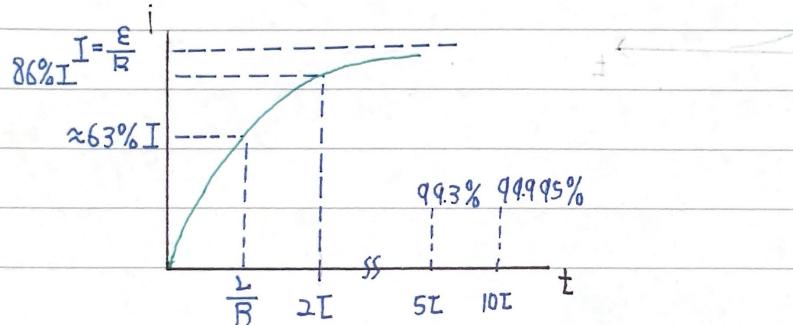
$$t \rightarrow \infty \quad i \rightarrow \frac{\mathcal{E}}{R} \quad \frac{di}{dt} \rightarrow 0$$



$$\text{when } \tau, \text{ time constant, } \Rightarrow t = \frac{\tau}{R}, \quad i = \left(1 - e^{-\frac{t}{\tau}} \right)$$


$$P = \mathcal{E}i = i^2 R + L i \frac{di}{dt}$$

current decay



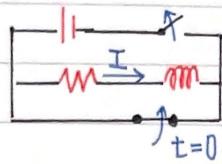


$$iR + L \frac{di}{dt} = 0 \quad I(t=0) = \frac{\epsilon}{R}$$

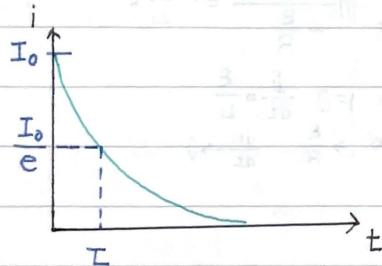
$$\frac{di}{dt} = -\frac{R}{L} i, \quad \frac{di}{i} = -\frac{R}{L} dt, \quad \int_{I_0}^i \frac{di'}{i'} = -\frac{R}{L} \int_0^t dt' \\ \ln \frac{i}{I_0} = -\frac{R}{L} t, \quad i = I_0 e^{-\frac{R}{L} t}$$




The L-C Circuit

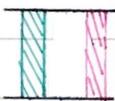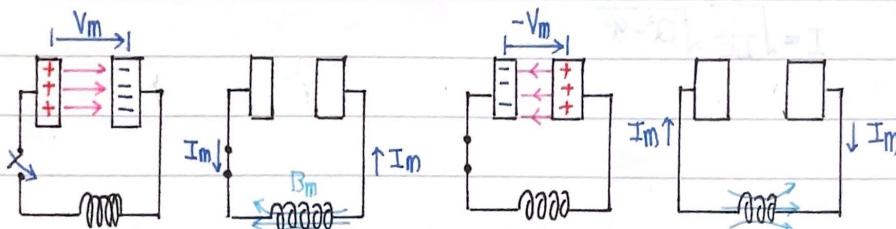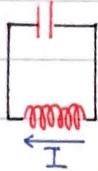

$$E = U_L + U_C$$

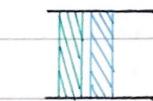

$$t = \frac{1}{k} T$$

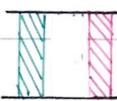

10

$$-\frac{dI}{dt} - \frac{I}{C} = 0$$

$$\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$$

$$U = U_E + U_B = \frac{q^2}{2C} + \frac{1}{2} L i^2 = \frac{Q_{max}^2}{2C}$$

$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{q^2}{2C} + \frac{1}{2} L j^2 \right) = \frac{q}{C} \frac{dq}{dt} + L j \frac{dj}{dt} = 0$$

$$\frac{d^2q}{dt^2} + \frac{1}{C}q = 0$$

$$\frac{d^2q}{dt^2} = -\frac{q}{2C} = -\omega^2 q \quad \omega^2 = \frac{1}{2C}$$

Let $g = e^{\lambda t}$, then $\lambda^2 e^{\lambda t} + \omega^2 e^{\lambda t} = 0$, $e^{\lambda t}(\lambda^2 + \omega^2) = 0$ $\because e^{\lambda t} \neq 0$, $\lambda^2 + \omega^2 = 0$

$$\lambda^2 = -\omega^2, \quad \lambda = \pm \omega i$$

$$q_1 = e^{i\omega t} = \cos \omega t + i \sin \omega t, \quad q = Q_{\max} \cos(\omega t + \phi)$$

$$j = \frac{dQ}{dt} = -\omega Q_{\max} \sin(\omega t + \phi) = -I_{\max} \sin(\omega t + \phi)$$

NO.

DATE / /

$$\begin{aligned} U &= U_B + U_E = \frac{1}{2} L i^2 + \frac{Q^2}{2C} = \frac{Q_{\max}^2}{2C} \\ &= \frac{Q_{\max}^2}{2C} \cos^2(\omega t) + \frac{1}{2} L I_{\max}^2 \sin^2(\omega t) \\ \Rightarrow \frac{Q_{\max}^2}{2C} &= \frac{L I_{\max}^2}{2} \end{aligned}$$

$$I = \sqrt{\frac{1}{2C}} \sqrt{Q^2 - Q^2}$$



$$\frac{Q_{\max}^2}{2C} = \frac{1}{2} L \left(\frac{\pi}{\omega} \right)^2 = \frac{1}{2} L \omega^2 \frac{\pi^2}{4} = \frac{1}{2} L \omega^2 \frac{\pi^2}{4}$$

$$Q_{\max}^2 = \frac{1}{2} L \omega^2 \frac{\pi^2}{4} = \left(\frac{1}{2} L \omega^2 \right) \frac{\pi^2}{4} = \frac{1}{2} L \omega^2 \frac{\pi^2}{4}$$

$$Q_{\max}^2 = \frac{1}{2} L \omega^2 \frac{\pi^2}{4}$$


$$Q_{\max}^2 = \frac{1}{2} L \omega^2 \frac{\pi^2}{4} = \frac{1}{2} L \omega^2 \frac{\pi^2}{4} = \frac{1}{2} L \omega^2 \frac{\pi^2}{4}$$

$$Q_{\max}^2 = \frac{1}{2} L \omega^2 \frac{\pi^2}{4} = \frac{1}{2} L \omega^2 \frac{\pi^2}{4} = \frac{1}{2} L \omega^2 \frac{\pi^2}{4}$$

$$(Q+10)(Q-10) = 0 \quad \text{or} \quad Q^2 + 10Q - 10Q - 100 = 0 \quad \Rightarrow \quad Q = 10$$

$$(Q+10)(Q-10) = 0 \quad \text{or} \quad Q^2 + 10Q - 10Q - 100 = 0 \quad \Rightarrow \quad Q = 10$$

The L-R-C Series Circuit

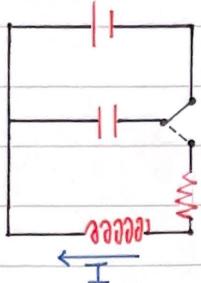

$$-IR - L \frac{di}{dt} - \frac{Q}{C} = 0, \quad \frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = 0$$

let $Q = Ae^{\lambda t}$, $A\lambda^2 e^{\lambda t} + \frac{R}{L} A\lambda e^{\lambda t} + \omega_0^2 A e^{\lambda t} = 0$
 $Ae^{\lambda t} (\lambda^2 + \frac{R}{L}\lambda + \omega_0^2) = 0$ and $\lambda^2 + \frac{R}{L}\lambda + \omega_0^2 = 0$

R small: underdamped

R large: overdamped

when $R^2 < \frac{4L}{C}$, $Q = Ae^{-\frac{R}{2L}t} \cos(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t + \phi)$

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$